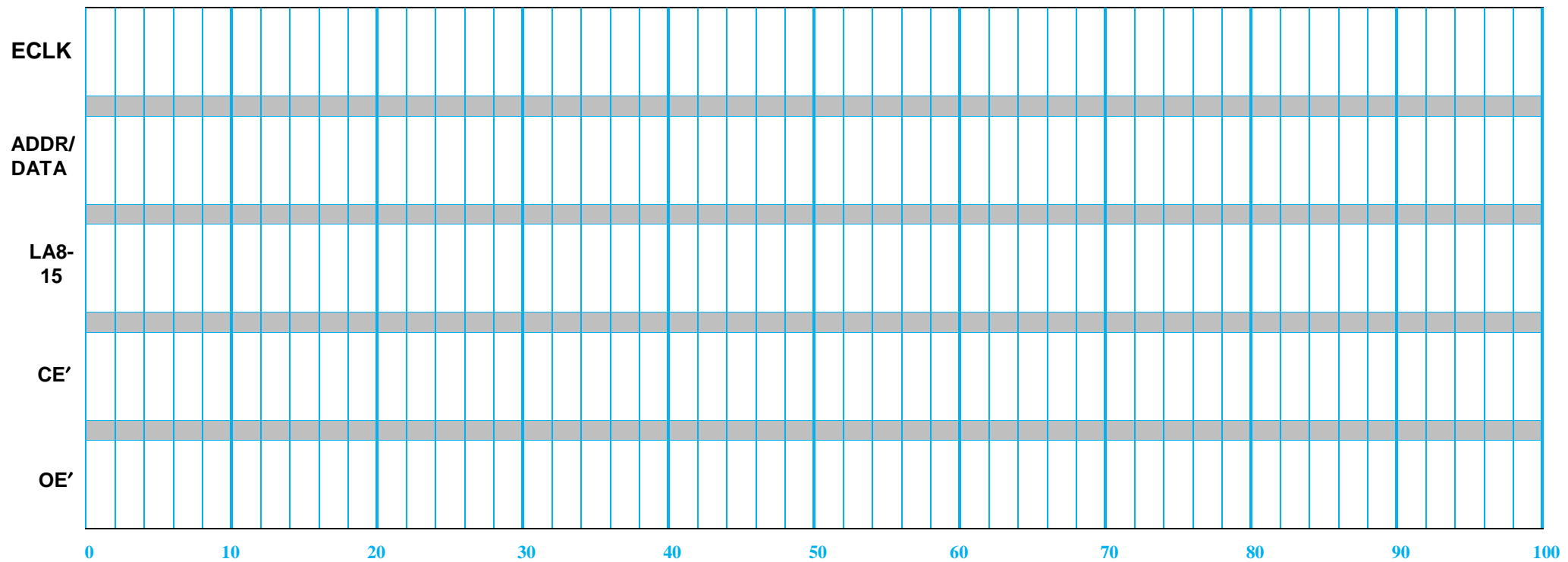


Homework Set 1 for Module 2 Problem #3 Worksheet – Completed by CN: \_\_\_\_ - \_\_\_\_

Maximum Bus Clock Speed for Given Components with No Stretch



Note: Scale is 2 ns/division – assume 0 ns rise/fall times